


VLSI DESIGN PROJECT

4-BIT CARRY LOOK-AHEAD ADDER

ARSHINI GOVINDU


2020102009

Block Structure

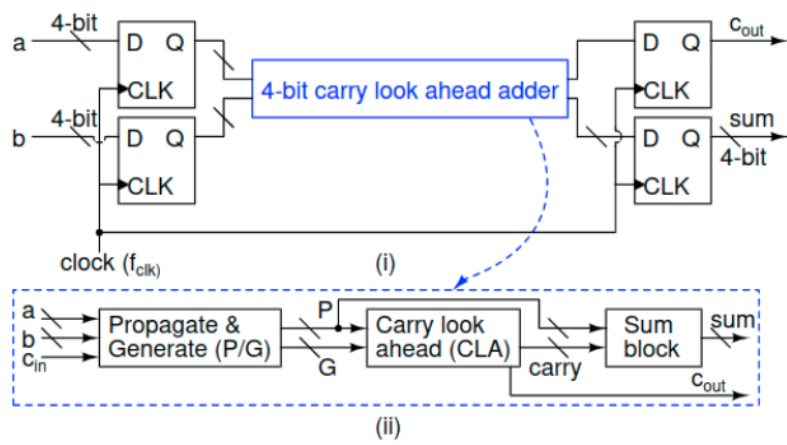


Design Details





Propagate and Generate Block

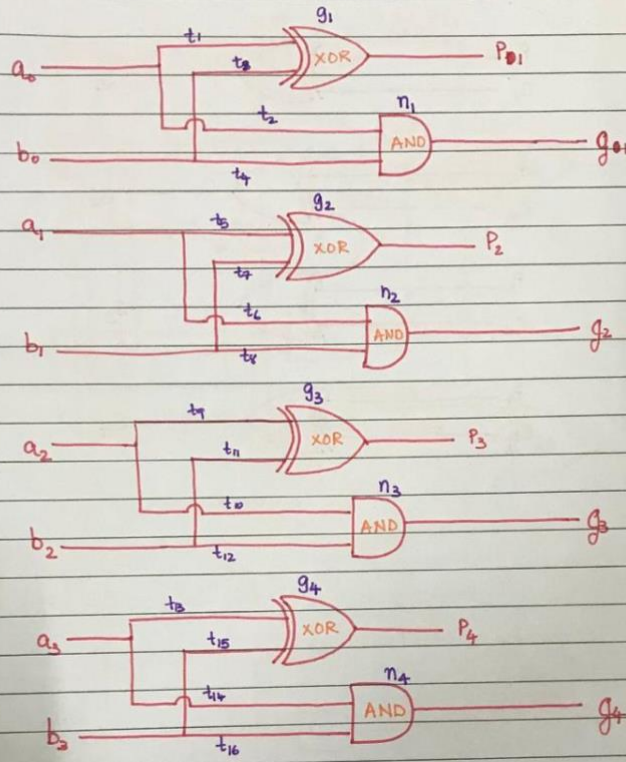




Carry Block



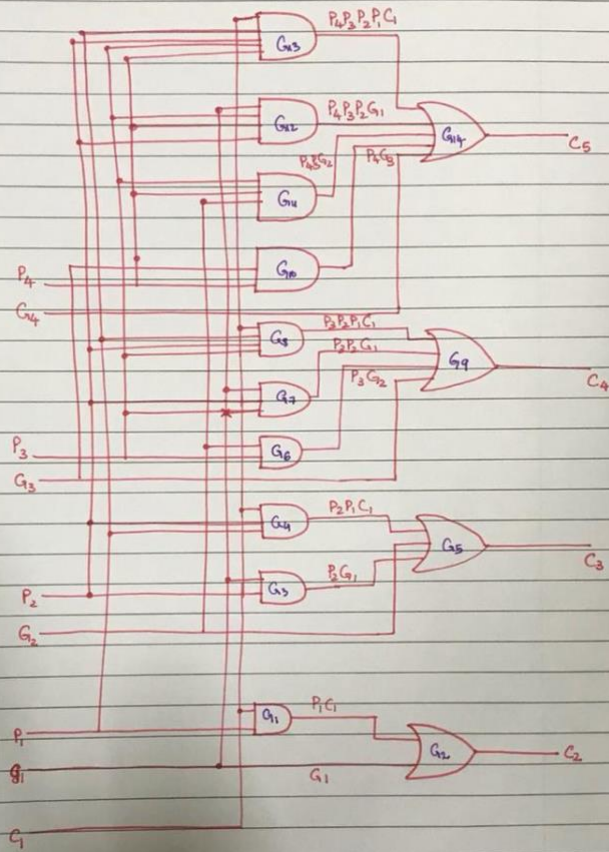





Sum Block

   
 





NGspice

   

   

   


  

   


MAGIC Layout


XOR Gate

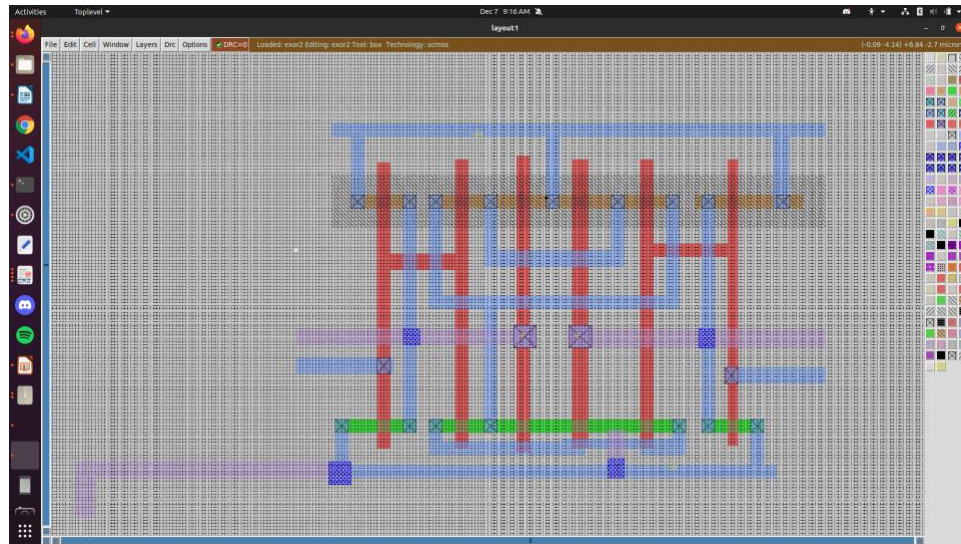

NOT Gate

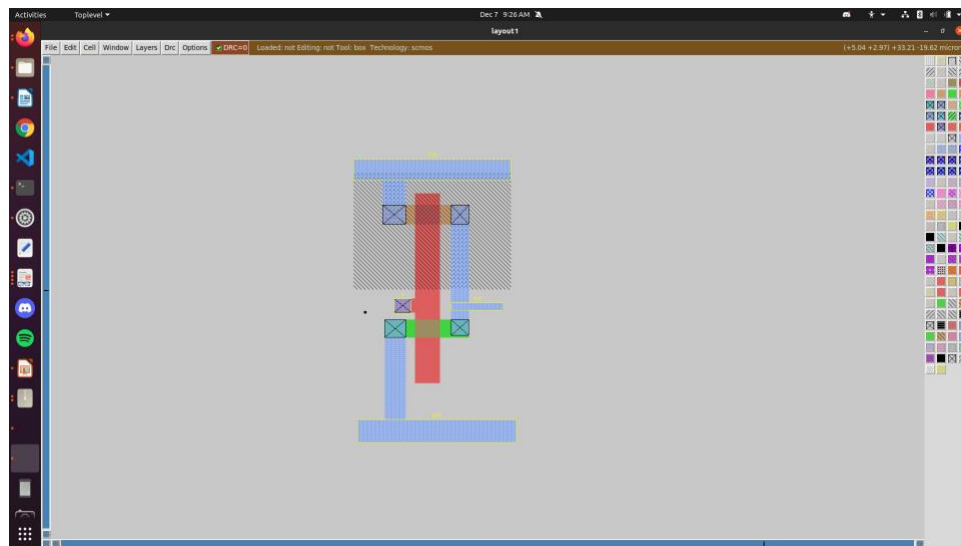


AND Gate

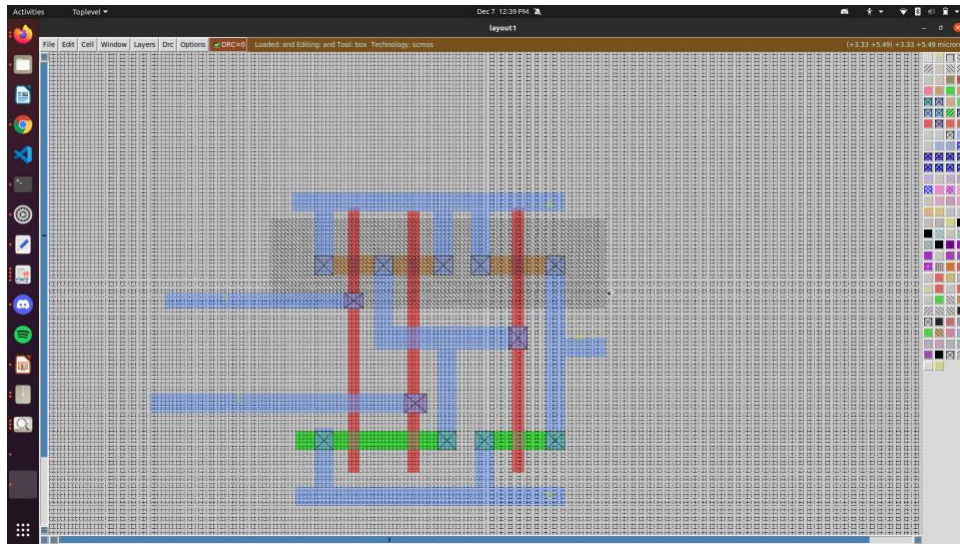


3-input AND Gate




4-input AND Gate

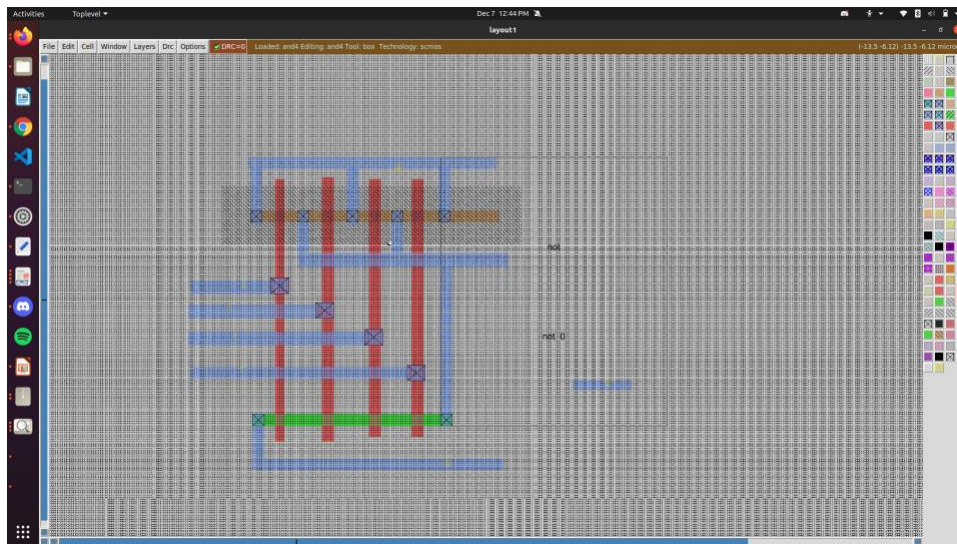


5-input AND Gate

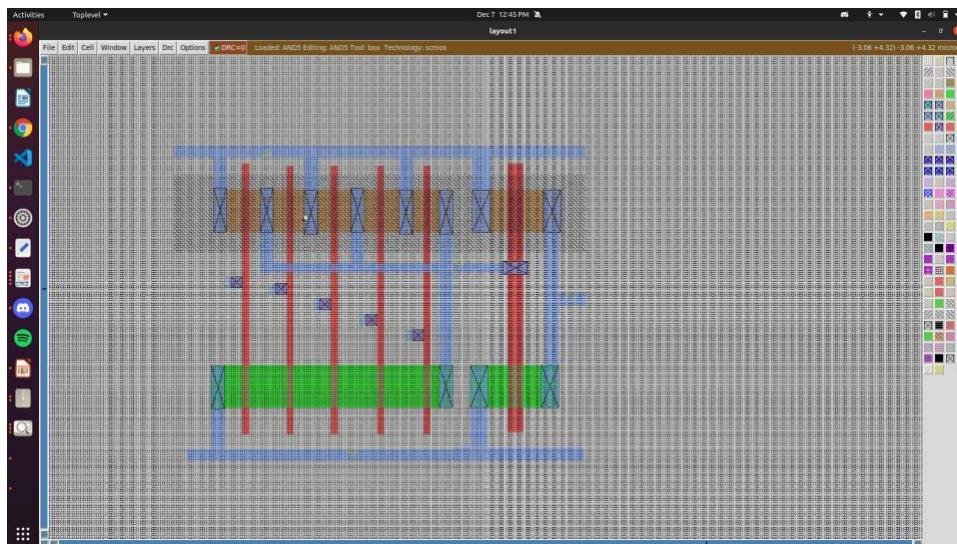


OR Gate

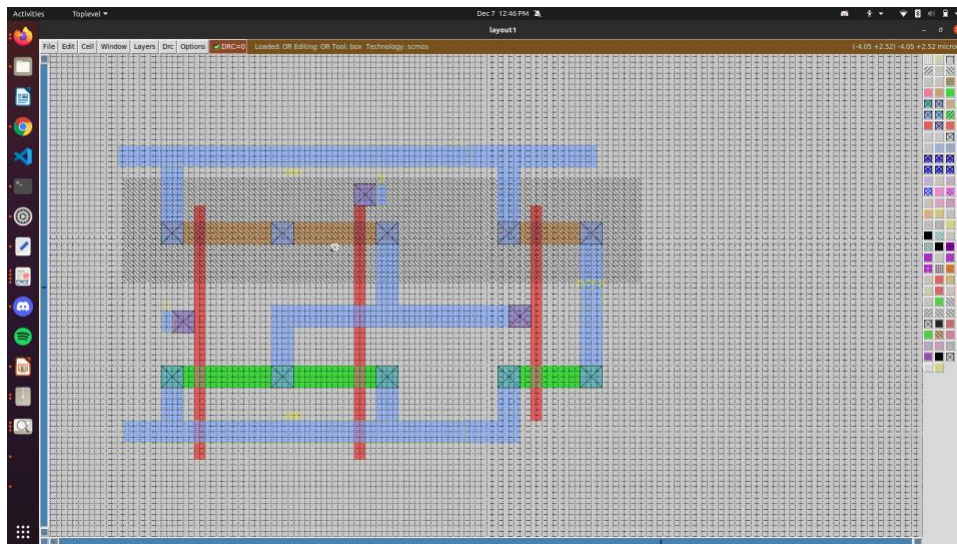


3-input OR Gate

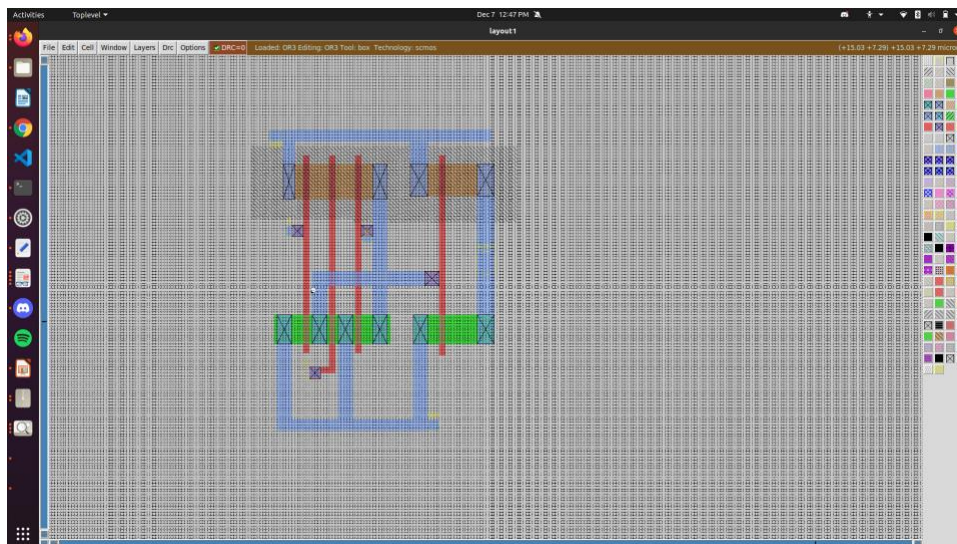

4-input OR Gate

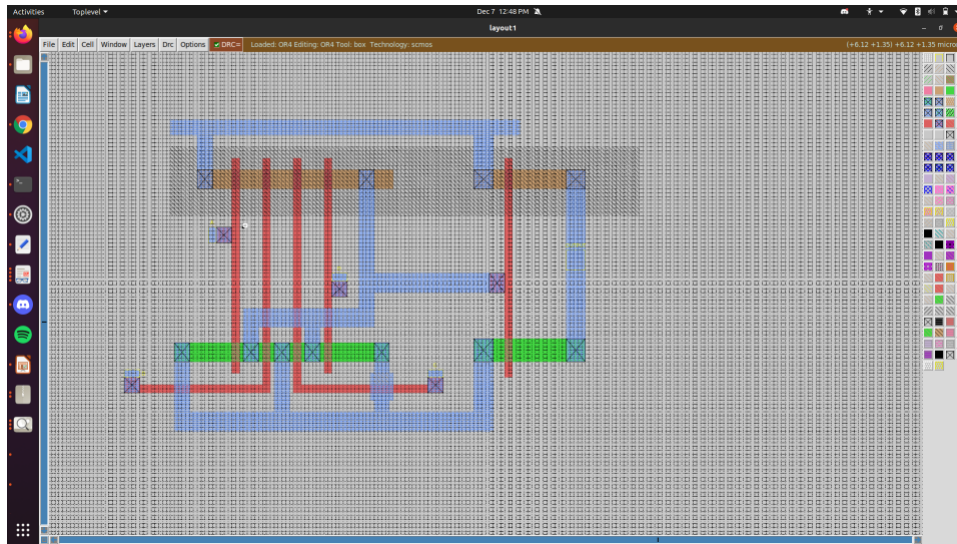

5-input OR Gate

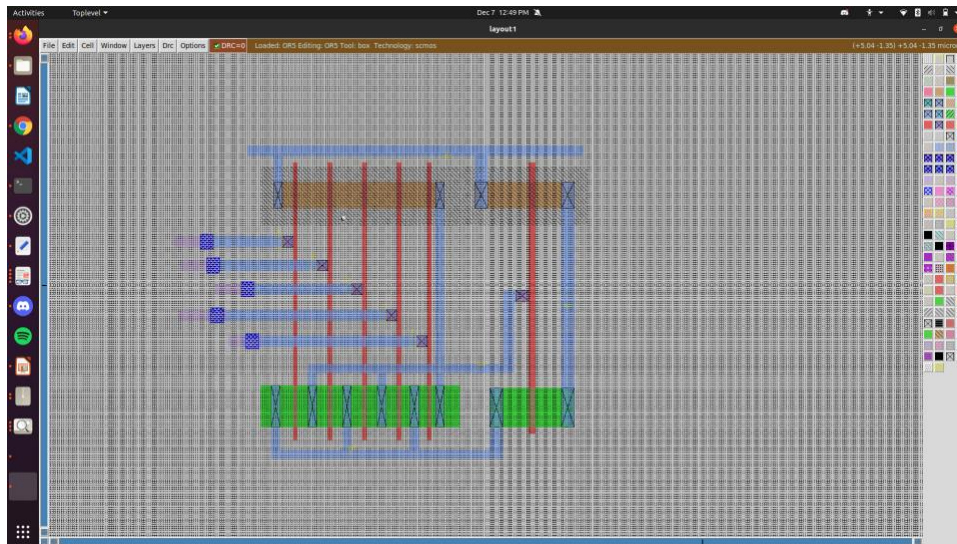

Pre-layout Netlist(Ngspice)

```
.include TSMC_180nm.txt
.global Gnd Vdd
.subckt exor 7 2 4 1 0
M001 3 2 1 1 CMOSP W = 3.6u L = 0.18u
M001 3 2 0 0 CMOSN W = 1.8u L = 0.18u
M002 5 4 1 1 CMOSP W = 3.6u L = 0.18u
M002 5 4 0 0 CMOSN W = 1.8u L = 0.18u
```

```

M003 6 2 1 1 CMOSP W = 3.6u L = 0.18u
M004 6 4 1 1 CMOSP W = 3.6u L = 0.18u
M005 7 3 6 1 CMOSP W = 3.6u L = 0.18u
M006 7 5 6 1 CMOSP W = 3.6u L = 0.18u
M003 7 2 8 0 CMOSN W = 1.8u L = 0.18u
M004 8 4 0 0 CMOSN W = 1.8u L = 0.18u
M005 7 3 9 0 CMOSN W = 1.8u L = 0.18u
M006 9 5 0 0 CMOSN W = 1.8u L = 0.18u
.ends exor

```

```

.subckt and 1 4 5 6 0
M000 2 4 6 6 CMOSP W=3.6u L=0.18u
M001 2 5 6 6 CMOSP W=3.6u L=0.18u
M002 1 2 6 6 CMOSP W=3.6u L=0.18u
M000 2 5 3 0 CMOSN W=1.8u L=0.18u
M001 3 4 0 0 CMOSN W=1.8u L=0.18u
M002 1 2 0 0 CMOSN W=1.8u L=0.18u
.ends and

```

```

.subckt or 1 2 3 6 0
M000 6 2 4 6 CMOSP W=3.6u L=0.18u
M001 4 3 5 6 CMOSP W=3.6u L=0.18u
M002 6 5 1 6 CMOSP W=3.6u L=0.18u
M000 0 3 5 0 CMOSN W=1.8u L=0.18u
M001 0 2 5 0 CMOSN W=1.8u L=0.18u
M002 0 5 1 0 CMOSN W=1.8u L=0.18u
.ends or

```

```

.subckt cla K P C G Vdd Gnd

```



```
xtemp t C P Vdd Gnd and
xfinal K t G Vdd Gnd or
.ends cla
```

```
Vdd Vdd Gnd 1.8V
```

```
*a = 1100
```

```
vin1 a0 0 pulse 1.8 0 0ns 100ps 100ps 19.9ns 40ns
```

```
vin2 a1 0 pulse 1.8 0 0ns 100ps 100ps 19.9ns 40ns
```

```
vin3 a2 0 pulse 0 1.8 0ns 100ps 100ps 19.9ns 40ns
```

```
vin4 a3 0 pulse 0 1.8 0ns 100ps 100ps 19.9ns 40ns
```

```
*b = 0101
```

```
vin5 b0 0 pulse 0 1.8 0ns 100ps 100ps 19.9ns 40ns
```

```
vin6 b1 0 pulse 1.8 0 0ns 100ps 100ps 19.9ns 40ns
```

```
vin7 b2 0 pulse 0 1.8 0ns 100ps 100ps 19.9ns 40ns
```

```
vin8 b3 0 pulse 1.8 0 0ns 100ps 100ps 19.9ns 40ns
```

```
xp0 P0 a0 b0 Vdd Gnd exor
```

```
xp1 P1 a1 b1 Vdd Gnd exor
```

```
xp2 P2 a2 b2 Vdd Gnd exor
```

```
xp3 P3 a3 b3 Vdd Gnd exor
```

```
xg0 G0 a0 b0 Vdd Gnd and
```

```
xg1 G1 a1 b1 Vdd Gnd and
```

```
xg2 G2 a2 b2 Vdd Gnd and
```

```
xg3 G3 a3 b3 Vdd Gnd and
```

```
xc1 c1 P0 0 G0 Vdd Gnd cla
```

```
xc2 c2 P1 C1 G1 Vdd Gnd cla
```

```
xc3 c3 P2 C2 G2 Vdd Gnd cla
```

```
xc4 c4 P3 C3 G3 Vdd Gnd cla
```

```
xs0 s0 P0 0 Vdd Gnd exor
```

```
xs1 s1 P1 C1 Vdd Gnd exor
```

```
xs2 s2 P2 C2 Vdd Gnd exor
```

```
xs3 s3 P3 C3 Vdd Gnd exor
```

```
.tran 0.1n 200n
```

```
.control
```

```
run
```

```
set color0=white
```

```
set color1=red
```

```
set xbrushwidth=3.5
```

```
set curplottitle="Arshini_2020102009"
```

```
plot G1
```

```
plot G2
```

```
plot G3
```

```
plot G4
```

```
plot C1
```

```
plot C2
```

```
plot C3
```

```
plot C4
```

```
plot s0
```

```
plot s1
```

```
plot s2
```

```
plot s3
```

```
.endc
```

Pre-layout Netlist(Ngspice)

```
* SPICE3 file created from Magic.ext - technology: scmos
.include ./TSMC_180nm.txt
.option scale=0.09u

Vpower vdd gnd 1.8

M1000 cla4_0/OR5_0/B cla4_0/and4_0/not_0/a_n19_n11# cla4_0/OR5_0/vdd
cla4_0/and4_0/not_0/w_n33_n4# pfet w=4 l=3
+ ad=32 pd=24 as=3653 ps=1674

M1001 cla4_0/OR5_0/B cla4_0/and4_0/not_0/a_n19_n11# cla2_0/and3_0/c
Gnd nfet w=4 l=3
+ ad=32 pd=24 as=4201 ps=1958

M1002 cla4_0/and4_0/a_n47_n81# cla4_0/and_0/a cla4_0/and4_0/gnd Gnd
nfet w=5 l=4
+ ad=85 pd=44 as=50 ps=30

M1003 cla4_0/and4_0/a_n25_n81# cla4_0/and4_0/b
cla4_0/and4_0/a_n47_n81# Gnd nfet w=5 l=5
+ ad=80 pd=42 as=0 ps=0

M1004 cla4_0/OR5_0/vdd cla4_0/and4_0/b cla4_0/and4_0/a_n47_10#
cla4_0/and4_0/w_n75_0# pfet w=5 l=5
+ ad=0 pd=0 as=155 ps=82

M1005 cla4_0/OR5_0/vdd cla4_0/and4_0/d cla4_0/and4_0/a_n47_10#
cla4_0/and4_0/w_n75_0# pfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1006 cla4_0/and4_0/a_n47_10# cla4_0/and4_0/d cla4_0/and4_0/a_n4_n81#
Gnd nfet w=5 l=5
+ ad=65 pd=36 as=70 ps=38

M1007 cla4_0/and4_0/a_n4_n81# cla4_0/and4_0/c cla4_0/and4_0/a_n25_n81#
Gnd nfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0
```

```

M1008 cla4_0/and4_0/a_n47_10# cla4_0/and_0/a cla4_0/OR5_0/vdd
cla4_0/and4_0/w_n75_0# pfet w=5 l=4
+ ad=0 pd=0 as=0 ps=0

M1009 cla4_0/and4_0/a_n47_10# cla4_0/and4_0/c cla4_0/OR5_0/vdd
cla4_0/and4_0/w_n75_0# pfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1010 cla4_0/OR5_0/C cla2_0/and3_0/c cla4_0/OR5_0/vdd
cla4_0/and3_0/not_0/w_n33_n4# pfet w=4 l=3
+ ad=32 pd=24 as=0 ps=0

M1011 cla4_0/OR5_0/C cla2_0/and3_0/c cla2_0/and3_0/c Gnd nfet w=4 l=3
+ ad=32 pd=24 as=0 ps=0

M1012 cla2_0/and3_0/c cla3_0/and_0/b cla4_0/OR5_0/vdd
cla4_0/and3_0/w_n75_n9# pfet w=5 l=5
+ ad=405 pd=222 as=0 ps=0

M1013 cla4_0/OR5_0/vdd cla4_0/and3_0/b cla2_0/and3_0/c
cla4_0/and3_0/w_n75_n9# pfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1014 cla2_0/and3_0/c cla4_0/and_0/a cla4_0/OR5_0/vdd
cla4_0/and3_0/w_n75_n9# pfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1015 cla4_0/and3_0/a_n29_n65# cla4_0/and3_0/b
cla4_0/and3_0/a_n50_n65# Gnd nfet w=5 l=5
+ ad=80 pd=42 as=80 ps=42

M1016 cla2_0/and3_0/c cla3_0/and_0/b cla4_0/and3_0/a_n29_n65# Gnd nfet
w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1017 cla4_0/and3_0/a_n50_n65# cla4_0/and_0/a cla2_0/and3_0/c Gnd nfet
w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1018 cla4_0/OR5_0/D cla4_0/and_0/a_n67_5# cla4_0/OR5_0/vdd
cla4_0/and_0/w_n91_n4# pfet w=5 l=3
+ ad=55 pd=32 as=0 ps=0

```

M1019 cla4_0/and_0/a_n67_5# cla4_0/and_0/a cla4_0/OR5_0/vdd
cla4_0/and_0/w_n91_n4# pfet w=5 l=3
+ ad=65 pd=36 as=0 ps=0

M1020 cla4_0/and_0/a_n67_n42# cla4_0/and_0/a cla2_0/and3_0/c Gnd nfet
w=5 l=3
+ ad=65 pd=36 as=0 ps=0

M1021 cla4_0/and_0/a_n67_5# cla4_0/and_0/b cla4_0/and_0/a_n67_n42# Gnd
nfet w=5 l=3
+ ad=50 pd=30 as=0 ps=0

M1022 cla4_0/OR5_0/D cla4_0/and_0/a_n67_5# cla2_0/and3_0/c Gnd nfet
w=5 l=3
+ ad=55 pd=32 as=0 ps=0

M1023 cla4_0/OR5_0/vdd cla4_0/and_0/b cla4_0/and_0/a_n67_5#
cla4_0/and_0/w_n91_n4# pfet w=5 l=3
+ ad=0 pd=0 as=0 ps=0

M1024 cla4_0/OR5_0/a_n21_5# cla4_0/OR5_0/A cla4_0/OR5_0/vdd
cla4_0/OR5_0/w_n38_n3# pfet w=12 l=2
+ ad=168 pd=52 as=0 ps=0

M1025 cla4_0/OR5_0/a_11_5# cla4_0/OR5_0/C cla4_0/OR5_0/a_n5_5#
cla4_0/OR5_0/w_n38_n3# pfet w=12 l=2
+ ad=168 pd=52 as=168 ps=52

M1026 cla2_0/and3_0/c cla4_0/OR5_0/B cla4_0/OR5_0/nout Gnd nfet w=19
l=2
+ ad=0 pd=0 as=779 ps=196

M1027 cla4_0/OR5_0/nout cla4_0/OR5_0/E cla4_0/OR5_0/a_27_5#
cla4_0/OR5_0/w_n38_n3# pfet w=12 l=2
+ ad=72 pd=36 as=144 ps=48

M1028 cla4_0/OR5_0/a_n5_5# cla4_0/OR5_0/B cla4_0/OR5_0/a_n21_5#
cla4_0/OR5_0/w_n38_n3# pfet w=12 l=2
+ ad=0 pd=0 as=0 ps=0

M1029 cla4_0/OR5_0/nout cla4_0/OR5_0/C cla2_0/and3_0/c Gnd nfet w=19
l=2
+ ad=0 pd=0 as=0 ps=0

```

M1030 cla4_0/OR5_0/a_27_5# cla4_0/OR5_0/D cla4_0/OR5_0/a_11_5#
cla4_0/OR5_0/w_n38_n3# pfet w=12 l=2
+ ad=0 pd=0 as=0 ps=0

M1031 cla4_0/OR5_0/nout cla4_0/OR5_0/A cla2_0/and3_0/c Gnd nfet w=19
l=2
+ ad=0 pd=0 as=0 ps=0

M1032 cout cla4_0/OR5_0/nout cla2_0/and3_0/c Gnd nfet w=18 l=3
+ ad=324 pd=72 as=0 ps=0

M1033 cout cla4_0/OR5_0/nout cla4_0/OR5_0/vdd cla4_0/OR5_0/w_n38_n3#
pfet w=12 l=3
+ ad=216 pd=60 as=0 ps=0

M1034 cla2_0/and3_0/c cla4_0/OR5_0/D cla4_0/OR5_0/nout Gnd nfet w=19
l=2
+ ad=0 pd=0 as=0 ps=0

M1035 cla4_0/OR5_0/nout cla4_0/OR5_0/E cla2_0/and3_0/c Gnd nfet w=19
l=2
+ ad=0 pd=0 as=0 ps=0

M1036 cla4_0/OR5_0/vdd cla2_0/and_0/b cla4_0/AND5_0/out
cla4_0/AND5_0/w_n59_n15# pfet w=19 l=3
+ ad=0 pd=0 as=873 ps=210

M1037 cla4_0/OR5_0/A cla4_0/AND5_0/out cla4_0/OR5_0/vdd
cla4_0/AND5_0/w_n59_n15# pfet w=19 l=7
+ ad=323 pd=72 as=0 ps=0

M1038 cla4_0/AND5_0/a_n5_n85# cla4_0/AND5_0/b cla4_0/AND5_0/a_n25_n85#
Gnd nfet w=19 l=3
+ ad=323 pd=72 as=323 ps=72

M1039 cla4_0/AND5_0/out cla2_0/and3_0/c cla4_0/OR5_0/vdd
cla4_0/AND5_0/w_n59_n15# pfet w=19 l=3
+ ad=0 pd=0 as=0 ps=0

M1040 cla4_0/AND5_0/a_n25_n85# cla4_0/and_0/a cla2_0/and3_0/c Gnd nfet
w=19 l=3
+ ad=0 pd=0 as=0 ps=0

```

M1041 cla4_0/AND5_0/out cla4_0/AND5_0/c cla4_0/OR5_0/vdd
cla4_0/AND5_0/w_n59_n15# pfet w=19 l=3
+ ad=0 pd=0 as=0 ps=0

M1042 cla4_0/AND5_0/out cla4_0/and_0/a cla4_0/OR5_0/vdd
cla4_0/AND5_0/w_n59_n15# pfet w=19 l=3
+ ad=0 pd=0 as=0 ps=0

M1043 cla4_0/OR5_0/A cla4_0/AND5_0/out cla2_0/and3_0/c Gnd nfet w=19
l=7
+ ad=304 pd=70 as=0 ps=0

M1044 cla4_0/OR5_0/vdd cla4_0/AND5_0/b cla4_0/AND5_0/out
cla4_0/AND5_0/w_n59_n15# pfet w=19 l=3
+ ad=0 pd=0 as=0 ps=0

M1045 cla4_0/AND5_0/a_15_n85# cla4_0/AND5_0/c cla4_0/AND5_0/a_n5_n85#
Gnd nfet w=19 l=3
+ ad=342 pd=74 as=0 ps=0

M1046 cla4_0/AND5_0/a_36_n85# cla2_0/and_0/b cla4_0/AND5_0/a_15_n85#
Gnd nfet w=19 l=3
+ ad=342 pd=74 as=0 ps=0

M1047 cla4_0/AND5_0/out cla2_0/and3_0/c cla4_0/AND5_0/a_36_n85# Gnd
nfet w=19 l=3
+ ad=190 pd=58 as=0 ps=0

M1048 cla3_0/and4_0/vout cla3_0/and4_0/not_0/a_n19_n11#
cla3_0/and_0/vdd cla3_0/and4_0/not_0/w_n33_n4# pfet w=4 l=3
+ ad=32 pd=24 as=487 ps=288

M1049 cla3_0/and4_0/vout cla3_0/and4_0/not_0/a_n19_n11#
cla2_0/and3_0/c Gnd nfet w=4 l=3
+ ad=32 pd=24 as=0 ps=0

M1050 cla3_0/and4_0/a_n47_n81# cla3_0/and_0/a cla3_0/and4_0/d Gnd nfet
w=5 l=4
+ ad=85 pd=44 as=50 ps=30

M1051 cla3_0/and4_0/a_n25_n81# cla3_0/and4_0/b
cla3_0/and4_0/a_n47_n81# Gnd nfet w=5 l=5
+ ad=80 pd=42 as=0 ps=0

M1052 cla3_0/and_0/vdd cla3_0/and4_0/b cla3_0/and4_0/a_n47_10#
cla3_0/and4_0/w_n75_0# pfet w=5 l=5
+ ad=0 pd=0 as=155 ps=82

M1053 cla3_0/and_0/vdd cla3_0/and4_0/d cla3_0/and4_0/a_n47_10#
cla3_0/and4_0/w_n75_0# pfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1054 cla3_0/and4_0/a_n47_10# cla3_0/and4_0/d cla3_0/and4_0/a_n4_n81#
Gnd nfet w=5 l=5
+ ad=65 pd=36 as=70 ps=38

M1055 cla3_0/and4_0/a_n4_n81# cla3_0/and4_0/c cla3_0/and4_0/a_n25_n81#
Gnd nfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1056 cla3_0/and4_0/a_n47_10# cla3_0/and_0/a cla3_0/and_0/vdd
cla3_0/and4_0/w_n75_0# pfet w=5 l=4
+ ad=0 pd=0 as=0 ps=0

M1057 cla3_0/and4_0/a_n47_10# cla3_0/and4_0/c cla3_0/and_0/vdd
cla3_0/and4_0/w_n75_0# pfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1058 cla3_0/and3_0/not_0/vout cla2_0/and3_0/c cla3_0/and_0/vdd
cla3_0/and3_0/not_0/w_n33_n4# pfet w=4 l=3
+ ad=32 pd=24 as=0 ps=0

M1059 cla3_0/and3_0/not_0/vout cla2_0/and3_0/c cla2_0/and3_0/c Gnd
nfet w=4 l=3
+ ad=32 pd=24 as=0 ps=0

M1060 cla2_0/and3_0/c cla3_0/and_0/b cla3_0/and_0/vdd
cla3_0/and3_0/w_n75_n9# pfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1061 cla3_0/and_0/vdd cla3_0/and4_0/b cla2_0/and3_0/c
cla3_0/and3_0/w_n75_n9# pfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1062 cla2_0/and3_0/c cla3_0/and_0/a cla3_0/and_0/vdd
cla3_0/and3_0/w_n75_n9# pfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1063 cla3_0/and3_0/a_n29_n65# cla3_0/and4_0/b
cla3_0/and3_0/a_n50_n65# Gnd nfet w=5 l=5
+ ad=80 pd=42 as=80 ps=42
M1064 cla2_0/and3_0/c cla3_0/and_0/b cla3_0/and3_0/a_n29_n65# Gnd nfet
w=5 l=5
+ ad=0 pd=0 as=0 ps=0
M1065 cla3_0/and3_0/a_n50_n65# cla3_0/and_0/a cla2_0/and3_0/c Gnd nfet
w=5 l=5
+ ad=0 pd=0 as=0 ps=0
M1066 cla3_0/and_0/out cla3_0/and_0/a_n67_5# cla3_0/and_0/vdd
cla3_0/and_0/w_n91_n4# pfet w=5 l=3
+ ad=55 pd=32 as=0 ps=0
M1067 cla3_0/and_0/a_n67_5# cla3_0/and_0/a cla3_0/and_0/vdd
cla3_0/and_0/w_n91_n4# pfet w=5 l=3
+ ad=65 pd=36 as=0 ps=0
M1068 cla3_0/and_0/a_n67_n42# cla3_0/and_0/a cla2_0/and3_0/c Gnd nfet
w=5 l=3
+ ad=65 pd=36 as=0 ps=0
M1069 cla3_0/and_0/a_n67_5# cla3_0/and_0/b cla3_0/and_0/a_n67_n42# Gnd
nfet w=5 l=3
+ ad=50 pd=30 as=0 ps=0
M1070 cla3_0/and_0/out cla3_0/and_0/a_n67_5# cla2_0/and3_0/c Gnd nfet
w=5 l=3
+ ad=55 pd=32 as=0 ps=0
M1071 cla3_0/and_0/vdd cla3_0/and_0/b cla3_0/and_0/a_n67_5#
cla3_0/and_0/w_n91_n4# pfet w=5 l=3
+ ad=0 pd=0 as=0 ps=0
M1072 s1 m1_n610_n2977# pblock_0/exor2_0/a_n24_n3#
pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=64 pd=48 as=124 ps=78
M1073 pblock_0/not_0/vout pblock_0/not_0/vdd cla2_0/and3_0/c Gnd nfet
w=4 l=4
+ ad=64 pd=48 as=0 ps=0

M1074 pblock_0/exor2_0/a_n5_n72# pblock_0/exor2_0/a_n10_n46# s1 Gnd
nfet w=4 l=4
+ ad=52 pd=34 as=60 ps=38

M1075 pblock_0/not_0/vout pblock_0/not_0/vdd VDD
pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=64 pd=48 as=693 ps=392

M1076 s1 pblock_0/not_0/vdd pblock_0/exor2_0/a_n36_n72# Gnd nfet w=4
l=4
+ ad=0 pd=0 as=72 ps=52

M1077 cla2_0/and3_0/c m1_n610_n2977# pblock_0/not_1/vout Gnd nfet w=4
l=3
+ ad=0 pd=0 as=64 ps=48

M1078 pblock_0/exor2_0/a_13_n72# pblock_0/exor2_0/a_7_n46#
pblock_0/exor2_0/a_n5_n72# Gnd nfet w=4 l=5
+ ad=64 pd=40 as=0 ps=0

M1079 pblock_0/exor2_0/a_n36_n72# m1_n610_n2977#
pblock_0/exor2_0/a_13_n72# Gnd nfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1080 VDD pblock_0/exor2_0/a_n10_n46# pblock_0/exor2_0/a_n24_n3#
pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1081 pblock_0/exor2_0/a_n24_n3# pblock_0/not_0/vdd s1
pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1082 VDD m1_n610_n2977# pblock_0/not_1/vout
pblock_0/exor2_0/w_n66_n9# pfet w=4 l=3
+ ad=0 pd=0 as=72 ps=52

M1083 pblock_0/exor2_0/a_n24_n3# pblock_0/exor2_0/a_7_n46# VDD
pblock_0/exor2_0/w_n66_n9# pfet w=4 l=5
+ ad=0 pd=0 as=0 ps=0

M1084 pblock_0/not_0/vout pblock_0/not_0/vdd pblock_0/not_0/vdd
pblock_0/not_0/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=36 ps=26

M1085 pblock_0/not_0/vout pblock_0/not_0/vdd pblock_0/not_0/gnd Gnd
nfet w=4 l=3
+ ad=0 pd=0 as=32 ps=24
M1086 pblock_0/not_1/vout m1_n610_n2977# pblock_0/not_1/vdd
pblock_0/not_1/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=36 ps=26
M1087 pblock_0/not_1/vout m1_n610_n2977# pblock_0/not_1/gnd Gnd nfet
w=4 l=3
+ ad=0 pd=0 as=32 ps=24
M1088 s2 cla3_0/and4_0/b pblock_1/exor2_0/a_n24_n3#
pblock_1/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=64 pd=48 as=124 ps=78
M1089 pblock_1/not_0/vout cla2_0/and_0/b cla2_0/and3_0/c Gnd nfet w=4
l=4
+ ad=64 pd=48 as=0 ps=0
M1090 pblock_1/exor2_0/a_n5_n72# pblock_1/exor2_0/a_n10_n46# s2 Gnd
nfet w=4 l=4
+ ad=52 pd=34 as=60 ps=38
M1091 pblock_1/not_0/vout cla2_0/and_0/b VDD
pblock_1/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=64 pd=48 as=0 ps=0
M1092 s2 cla2_0/and_0/b pblock_1/exor2_0/a_n36_n72# Gnd nfet w=4 l=4
+ ad=0 pd=0 as=72 ps=52
M1093 cla2_0/and3_0/c cla3_0/and4_0/b pblock_1/not_1/vout Gnd nfet w=4
l=3
+ ad=0 pd=0 as=64 ps=48
M1094 pblock_1/exor2_0/a_13_n72# pblock_1/exor2_0/a_7_n46#
pblock_1/exor2_0/a_n5_n72# Gnd nfet w=4 l=5
+ ad=64 pd=40 as=0 ps=0
M1095 pblock_1/exor2_0/a_n36_n72# cla3_0/and4_0/b
pblock_1/exor2_0/a_13_n72# Gnd nfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1096 VDD pblock_1/exor2_0/a_n10_n46# pblock_1/exor2_0/a_n24_n3#
pblock_1/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1097 pblock_1/exor2_0/a_n24_n3# cla2_0/and_0/b s2
pblock_1/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1098 VDD cla3_0/and4_0/b pblock_1/not_1/vout
pblock_1/exor2_0/w_n66_n9# pfet w=4 l=3
+ ad=0 pd=0 as=72 ps=52

M1099 pblock_1/exor2_0/a_n24_n3# pblock_1/exor2_0/a_7_n46# VDD
pblock_1/exor2_0/w_n66_n9# pfet w=4 l=5
+ ad=0 pd=0 as=0 ps=0

M1100 pblock_1/not_0/vout cla2_0/and_0/b pblock_1/not_0/vdd
pblock_1/not_0/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=36 ps=26

M1101 pblock_1/not_0/vout cla2_0/and_0/b pblock_1/not_0/gnd Gnd nfet
w=4 l=3
+ ad=0 pd=0 as=32 ps=24

M1102 pblock_1/not_1/vout cla3_0/and4_0/b pblock_1/not_1/vdd
pblock_1/not_1/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=36 ps=26

M1103 pblock_1/not_1/vout cla3_0/and4_0/b pblock_1/not_1/gnd Gnd nfet
w=4 l=3
+ ad=0 pd=0 as=32 ps=24

M1104 s3 cla3_0/and_0/a pblock_2/exor2_0/a_n24_n3#
pblock_2/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=64 pd=48 as=124 ps=78

M1105 pblock_2/not_0/vout cla2_0/NOR3_0/OUTPUT cla2_0/and3_0/c Gnd
nfet w=4 l=4
+ ad=64 pd=48 as=0 ps=0

M1106 pblock_2/exor2_0/a_n5_n72# pblock_2/exor2_0/a_n10_n46# s3 Gnd
nfet w=4 l=4
+ ad=52 pd=34 as=60 ps=38

M1107 pblock_2/not_0/vout cla2_0/NOR3_0/OUTPUT pblock_2/exor2_0/vdd
 pblock_2/exor2_0/w_n66_n9# pfet w=4 l=4
 + ad=64 pd=48 as=164 ps=106

M1108 s3 cla2_0/NOR3_0/OUTPUT pblock_2/exor2_0/a_n36_n72# Gnd nfet w=4
 l=4
 + ad=0 pd=0 as=72 ps=52

M1109 cla2_0/and3_0/c cla3_0/and_0/a pblock_2/not_1/vout Gnd nfet w=4
 l=3
 + ad=0 pd=0 as=64 ps=48

M1110 pblock_2/exor2_0/a_13_n72# pblock_2/exor2_0/a_7_n46#
 pblock_2/exor2_0/a_n5_n72# Gnd nfet w=4 l=5
 + ad=64 pd=40 as=0 ps=0

M1111 pblock_2/exor2_0/a_n36_n72# cla3_0/and_0/a
 pblock_2/exor2_0/a_13_n72# Gnd nfet w=4 l=4
 + ad=0 pd=0 as=0 ps=0

M1112 pblock_2/exor2_0/vdd pblock_2/exor2_0/a_n10_n46#
 pblock_2/exor2_0/a_n24_n3# pblock_2/exor2_0/w_n66_n9# pfet w=4 l=4
 + ad=0 pd=0 as=0 ps=0

M1113 pblock_2/exor2_0/a_n24_n3# cla2_0/NOR3_0/OUTPUT s3
 pblock_2/exor2_0/w_n66_n9# pfet w=4 l=4
 + ad=0 pd=0 as=0 ps=0

M1114 pblock_2/exor2_0/vdd cla3_0/and_0/a pblock_2/not_1/vout
 pblock_2/exor2_0/w_n66_n9# pfet w=4 l=3
 + ad=0 pd=0 as=72 ps=52

M1115 pblock_2/exor2_0/a_n24_n3# pblock_2/exor2_0/a_7_n46#
 pblock_2/exor2_0/vdd pblock_2/exor2_0/w_n66_n9# pfet w=4 l=5
 + ad=0 pd=0 as=0 ps=0

M1116 pblock_2/not_0/vout cla2_0/NOR3_0/OUTPUT pblock_2/not_0/vdd
 pblock_2/not_0/w_n33_n4# pfet w=4 l=3
 + ad=0 pd=0 as=36 ps=26

M1117 pblock_2/not_0/vout cla2_0/NOR3_0/OUTPUT pblock_2/not_0/gnd Gnd
 nfet w=4 l=3
 + ad=0 pd=0 as=32 ps=24

M1118 pblock_2/not_1/vout cla3_0/and_0/a pblock_2/not_1/vdd
pblock_2/not_1/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=36 ps=26

M1119 pblock_2/not_1/vout cla3_0/and_0/a pblock_2/not_1/gnd Gnd nfet
w=4 l=3
+ ad=0 pd=0 as=32 ps=24

M1120 cla2_0/and3_0/not_0/vout cla2_0/and3_0/c VDD
cla2_0/and3_0/not_0/w_n33_n4# pfet w=4 l=3
+ ad=32 pd=24 as=0 ps=0

M1121 cla2_0/and3_0/not_0/vout cla2_0/and3_0/c cla2_0/and3_0/c Gnd
nfet w=4 l=3
+ ad=32 pd=24 as=0 ps=0

M1122 cla2_0/and3_0/c cla2_0/and3_0/c VDD cla2_0/and3_0/w_n75_n9# pfet
w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1123 VDD cla2_0/and_0/a cla2_0/and3_0/c cla2_0/and3_0/w_n75_n9# pfet
w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1124 cla2_0/and3_0/c cla2_0/and3_0/a VDD cla2_0/and3_0/w_n75_n9# pfet
w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1125 cla2_0/and3_0/a_n29_n65# cla2_0/and_0/a cla2_0/and3_0/a_n50_n65#
Gnd nfet w=5 l=5
+ ad=80 pd=42 as=80 ps=42

M1126 cla2_0/and3_0/c cla2_0/and3_0/c cla2_0/and3_0/a_n29_n65# Gnd
nfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1127 cla2_0/and3_0/a_n50_n65# cla2_0/and3_0/a cla2_0/and3_0/c Gnd
nfet w=5 l=5
+ ad=0 pd=0 as=0 ps=0

M1128 cla2_0/NOR3_0/c cla2_0/and_0/a_n67_5# cla2_0/and_0/vdd
cla2_0/and_0/w_n91_n4# pfet w=5 l=3
+ ad=55 pd=32 as=145 ps=88

M1129 cla2_0/and_0/a_n67_5# cla2_0/and_0/a cla2_0/and_0/vdd
cla2_0/and_0/w_n91_n4# pfet w=5 l=3
+ ad=65 pd=36 as=0 ps=0

M1130 cla2_0/and_0/a_n67_n42# cla2_0/and_0/a cla2_0/and3_0/c Gnd nfet
w=5 l=3
+ ad=65 pd=36 as=0 ps=0

M1131 cla2_0/and_0/a_n67_5# cla2_0/and_0/b cla2_0/and_0/a_n67_n42# Gnd
nfet w=5 l=3
+ ad=50 pd=30 as=0 ps=0

M1132 cla2_0/NOR3_0/c cla2_0/and_0/a_n67_5# cla2_0/and3_0/c Gnd nfet
w=5 l=3
+ ad=55 pd=32 as=0 ps=0

M1133 cla2_0/and_0/vdd cla2_0/and_0/b cla2_0/and_0/a_n67_5#
cla2_0/and_0/w_n91_n4# pfet w=5 l=3
+ ad=0 pd=0 as=0 ps=0

M1134 cla2_0/NOR3_0/OUTPUT cla2_0/NOR3_0/a_n1_n18# cla2_0/and3_0/c Gnd
nfet w=10 l=2
+ ad=170 pd=54 as=0 ps=0

M1135 cla2_0/and3_0/c cla2_0/m2_n103_n35# cla2_0/NOR3_0/a_n1_n18# Gnd
nfet w=10 l=2
+ ad=0 pd=0 as=170 ps=74

M1136 cla2_0/NOR3_0/a_n1_n18# cla2_0/NOR3_0/c cla2_0/NOR3_0/a_8_32#
cla2_0/NOR3_0/w_n21_25# pfet w=12 l=2
+ ad=108 pd=42 as=84 ps=38

M1137 cla2_0/NOR3_0/OUTPUT cla2_0/NOR3_0/a_n1_n18# VDD
cla2_0/NOR3_0/w_n21_25# pfet w=11 l=2
+ ad=187 pd=56 as=0 ps=0

M1138 cla2_0/NOR3_0/a_n1_32# cla3_0/and_0/b VDD
cla2_0/NOR3_0/w_n21_25# pfet w=12 l=2
+ ad=84 pd=38 as=0 ps=0

M1139 cla2_0/NOR3_0/a_8_32# cla2_0/m2_n103_n35# cla2_0/NOR3_0/a_n1_32#
cla2_0/NOR3_0/w_n21_25# pfet w=12 l=2
+ ad=0 pd=0 as=0 ps=0

M1140 cla2_0/NOR3_0/a_n1_n18# cla3_0/and_0/b cla2_0/and3_0/c Gnd nfet
w=10 l=2
+ ad=0 pd=0 as=0 ps=0
M1141 cla2_0/NOR3_0/a_n1_n18# cla2_0/NOR3_0/c cla2_0/and3_0/c Gnd nfet
w=10 l=2
+ ad=0 pd=0 as=0 ps=0
M1142 s4 cla4_0/and_0/a pblock_3/exor2_0/a_n24_n3#
pblock_3/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=136 pd=100 as=124 ps=78
M1143 pblock_3/not_0/vout m1_981_n2115# cla2_0/and3_0/c Gnd nfet w=4
l=4
+ ad=64 pd=48 as=0 ps=0
M1144 pblock_3/exor2_0/a_n5_n72# pblock_3/exor2_0/a_n10_n46# s4 Gnd
nfet w=4 l=4
+ ad=52 pd=34 as=124 ps=86
M1145 pblock_3/not_0/vout m1_981_n2115# pblock_3/exor2_0/vdd
pblock_3/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=64 pd=48 as=164 ps=106
M1146 s4 m1_981_n2115# pblock_3/exor2_0/a_n36_n72# Gnd nfet w=4 l=4
+ ad=0 pd=0 as=72 ps=52
M1147 cla2_0/and3_0/c cla4_0/and_0/a s4 Gnd nfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0
M1148 pblock_3/exor2_0/a_13_n72# pblock_3/exor2_0/a_7_n46#
pblock_3/exor2_0/a_n5_n72# Gnd nfet w=4 l=5
+ ad=64 pd=40 as=0 ps=0
M1149 pblock_3/exor2_0/a_n36_n72# cla4_0/and_0/a
pblock_3/exor2_0/a_13_n72# Gnd nfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0
M1150 pblock_3/exor2_0/vdd pblock_3/exor2_0/a_n10_n46#
pblock_3/exor2_0/a_n24_n3# pblock_3/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0
M1151 pblock_3/exor2_0/a_n24_n3# m1_981_n2115# s4
pblock_3/exor2_0/w_n66_n9# pfet w=4 l=4

+ ad=0 pd=0 as=0 ps=0

M1152 pblock_3/exor2_0/vdd cla4_0/and_0/a s4
pblock_3/exor2_0/w_n66_n9# pfet w=4 l=3

+ ad=0 pd=0 as=0 ps=0

M1153 pblock_3/exor2_0/a_n24_n3# pblock_3/exor2_0/a_7_n46#
pblock_3/exor2_0/vdd pblock_3/exor2_0/w_n66_n9# pfet w=4 l=5

+ ad=0 pd=0 as=0 ps=0

M1154 pblock_3/not_0/vout m1_981_n2115# pblock_3/not_0/vdd
pblock_3/not_0/w_n33_n4# pfet w=4 l=3

+ ad=0 pd=0 as=36 ps=26

M1155 pblock_3/not_0/vout m1_981_n2115# pblock_3/not_0/gnd Gnd nfet
w=4 l=3

+ ad=0 pd=0 as=32 ps=24

M1156 s4 cla4_0/and_0/a pblock_3/not_1/vdd pblock_3/not_1/w_n33_n4#
pfet w=4 l=3

+ ad=0 pd=0 as=36 ps=26

M1157 s4 cla4_0/and_0/a pblock_3/not_1/gnd Gnd nfet w=4 l=3

+ ad=0 pd=0 as=32 ps=24

M1158 cla2_0/and_0/b pblock_0/and_0/a_n67_5# cla4_0/OR5_0/vdd
pblock_0/and_0/w_n91_n4# pfet w=5 l=3

+ ad=55 pd=32 as=0 ps=0

M1159 pblock_0/and_0/a_n67_5# aa cla4_0/OR5_0/vdd
pblock_0/and_0/w_n91_n4# pfet w=5 l=3

+ ad=65 pd=36 as=0 ps=0

M1160 pblock_0/and_0/a_n67_n42# aa cla2_0/and3_0/c Gnd nfet w=5 l=3

+ ad=65 pd=36 as=0 ps=0

M1161 pblock_0/and_0/a_n67_5# ba pblock_0/and_0/a_n67_n42# Gnd nfet
w=5 l=3

+ ad=50 pd=30 as=0 ps=0

M1162 cla2_0/and_0/b pblock_0/and_0/a_n67_5# cla2_0/and3_0/c Gnd nfet
w=5 l=3

+ ad=55 pd=32 as=0 ps=0

M1163 cla4_0/OR5_0/vdd ba pdblock_0/and_0/a_n67_5#
pdblock_0/and_0/w_n91_n4# pfet w=5 l=3
+ ad=0 pd=0 as=0 ps=0

M1164 pdblock_0/pblock_0/not_1/vout ba
pdblock_0/pblock_0/exor2_0/a_n24_n3#
pdblock_0/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=136 pd=100 as=124 ps=78

M1165 pdblock_0/pblock_0/not_0/vout aa cla2_0/and3_0/c Gnd nfet w=4
l=4
+ ad=64 pd=48 as=0 ps=0

M1166 pdblock_0/pblock_0/exor2_0/a_n5_n72#
pdblock_0/pblock_0/exor2_0/a_n10_n46# pdblock_0/pblock_0/not_1/vout
Gnd nfet w=4 l=4
+ ad=52 pd=34 as=124 ps=86

M1167 pdblock_0/pblock_0/not_0/vout aa cla4_0/OR5_0/vdd
pdblock_0/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=64 pd=48 as=0 ps=0

M1168 pdblock_0/pblock_0/not_1/vout aa
pdblock_0/pblock_0/exor2_0/a_n36_n72# Gnd nfet w=4 l=4
+ ad=0 pd=0 as=72 ps=52

M1169 cla2_0/and3_0/c ba pdblock_0/pblock_0/not_1/vout Gnd nfet w=4
l=3
+ ad=0 pd=0 as=0 ps=0

M1170 pdblock_0/pblock_0/exor2_0/a_13_n72#
pdblock_0/pblock_0/exor2_0/a_7_n46#
pdblock_0/pblock_0/exor2_0/a_n5_n72# Gnd nfet w=4 l=5
+ ad=64 pd=40 as=0 ps=0

M1171 pdblock_0/pblock_0/exor2_0/a_n36_n72# ba
pdblock_0/pblock_0/exor2_0/a_13_n72# Gnd nfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1172 cla4_0/OR5_0/vdd pdblock_0/pblock_0/exor2_0/a_n10_n46#
pdblock_0/pblock_0/exor2_0/a_n24_n3#
pdblock_0/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1173 pdblock_0/pblock_0/exor2_0/a_n24_n3# aa
pdblock_0/pblock_0/not_1/vout pdblock_0/pblock_0/exor2_0/w_n66_n9#
pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0
M1174 cla4_0/OR5_0/vdd ba pdblock_0/pblock_0/not_1/vout
pdblock_0/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0
M1175 pdblock_0/pblock_0/exor2_0/a_n24_n3#
pdblock_0/pblock_0/exor2_0/a_7_n46# cla4_0/OR5_0/vdd
pdblock_0/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=5
+ ad=0 pd=0 as=0 ps=0
M1176 pdblock_0/pblock_0/not_0/vout aa cla4_0/OR5_0/vdd
pdblock_0/pblock_0/not_0/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0
M1177 pdblock_0/pblock_0/not_0/vout aa cla2_0/and3_0/c Gnd nfet w=4
l=3
+ ad=0 pd=0 as=0 ps=0
M1178 pdblock_0/pblock_0/not_1/vout ba cla4_0/OR5_0/vdd
pdblock_0/pblock_0/not_1/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0
M1179 pdblock_0/pblock_0/not_1/vout ba cla2_0/and3_0/c Gnd nfet w=4
l=3
+ ad=0 pd=0 as=0 ps=0
M1180 cla3_0/and_0/b pdblock_1/and_0/a_n67_5# cla4_0/OR5_0/vdd
pdblock_1/and_0/w_n91_n4# pfet w=5 l=3
+ ad=55 pd=32 as=0 ps=0
M1181 pdblock_1/and_0/a_n67_5# ab cla4_0/OR5_0/vdd
pdblock_1/and_0/w_n91_n4# pfet w=5 l=3
+ ad=65 pd=36 as=0 ps=0
M1182 pdblock_1/and_0/a_n67_n42# ab cla2_0/and3_0/c Gnd nfet w=5 l=3
+ ad=65 pd=36 as=0 ps=0
M1183 pdblock_1/and_0/a_n67_5# bb pdblock_1/and_0/a_n67_n42# Gnd nfet
w=5 l=3
+ ad=50 pd=30 as=0 ps=0

M1184 cla3_0/and_0/b pdblock_1/and_0/a_n67_5# cla2_0/and3_0/c Gnd nfet
w=5 l=3

+ ad=55 pd=32 as=0 ps=0

M1185 cla4_0/OR5_0/vdd bb pdblock_1/and_0/a_n67_5#
pdblock_1/and_0/w_n91_n4# pfet w=5 l=3

+ ad=0 pd=0 as=0 ps=0

M1186 pdblock_1/pblock_0/not_1/vout bb
pdblock_1/pblock_0/exor2_0/a_n24_n3#
pdblock_1/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4

+ ad=136 pd=100 as=124 ps=78

M1187 pdblock_1/pblock_0/not_0/vout ab cla2_0/and3_0/c Gnd nfet w=4
l=4

+ ad=64 pd=48 as=0 ps=0

M1188 pdblock_1/pblock_0/exor2_0/a_n5_n72#
pdblock_1/pblock_0/exor2_0/a_n10_n46# pdblock_1/pblock_0/not_1/vout
Gnd nfet w=4 l=4

+ ad=52 pd=34 as=124 ps=86

M1189 pdblock_1/pblock_0/not_0/vout ab cla4_0/OR5_0/vdd
pdblock_1/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4

+ ad=64 pd=48 as=0 ps=0

M1190 pdblock_1/pblock_0/not_1/vout ab
pdblock_1/pblock_0/exor2_0/a_n36_n72# Gnd nfet w=4 l=4

+ ad=0 pd=0 as=72 ps=52

M1191 cla2_0/and3_0/c bb pdblock_1/pblock_0/not_1/vout Gnd nfet w=4
l=3

+ ad=0 pd=0 as=0 ps=0

M1192 pdblock_1/pblock_0/exor2_0/a_13_n72#
pdblock_1/pblock_0/exor2_0/a_7_n46#
pdblock_1/pblock_0/exor2_0/a_n5_n72# Gnd nfet w=4 l=5

+ ad=64 pd=40 as=0 ps=0

M1193 pdblock_1/pblock_0/exor2_0/a_n36_n72# bb
pdblock_1/pblock_0/exor2_0/a_13_n72# Gnd nfet w=4 l=4

+ ad=0 pd=0 as=0 ps=0

M1194 cla4_0/OR5_0/vdd pdblock_1/pblock_0/exor2_0/a_n10_n46#
pdblock_1/pblock_0/exor2_0/a_n24_n3#
pdblock_1/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0
M1195 pdblock_1/pblock_0/exor2_0/a_n24_n3# ab
pdblock_1/pblock_0/not_1/vout pdblock_1/pblock_0/exor2_0/w_n66_n9#
pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0
M1196 cla4_0/OR5_0/vdd bb pdblock_1/pblock_0/not_1/vout
pdblock_1/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0
M1197 pdblock_1/pblock_0/exor2_0/a_n24_n3#
pdblock_1/pblock_0/exor2_0/a_7_n46# cla4_0/OR5_0/vdd
pdblock_1/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=5
+ ad=0 pd=0 as=0 ps=0
M1198 pdblock_1/pblock_0/not_0/vout ab cla4_0/OR5_0/vdd
pdblock_1/pblock_0/not_0/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0
M1199 pdblock_1/pblock_0/not_0/vout ab cla2_0/and3_0/c Gnd nfet w=4
l=3
+ ad=0 pd=0 as=0 ps=0
M1200 pdblock_1/pblock_0/not_1/vout bb cla4_0/OR5_0/vdd
pdblock_1/pblock_0/not_1/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0
M1201 pdblock_1/pblock_0/not_1/vout bb cla2_0/and3_0/c Gnd nfet w=4
l=3
+ ad=0 pd=0 as=0 ps=0
M1202 cla4_0/and_0/b pdblock_2/and_0/a_n67_5# cla4_0/OR5_0/vdd
pdblock_2/and_0/w_n91_n4# pfet w=5 l=3
+ ad=55 pd=32 as=0 ps=0
M1203 pdblock_2/and_0/a_n67_5# ac cla4_0/OR5_0/vdd
pdblock_2/and_0/w_n91_n4# pfet w=5 l=3
+ ad=65 pd=36 as=0 ps=0
M1204 pdblock_2/and_0/a_n67_n42# ac cla2_0/and3_0/c Gnd nfet w=5 l=3

+ ad=65 pd=36 as=0 ps=0

M1205 pdblock_2/and_0/a_n67_5# bc pdblock_2/and_0/a_n67_n42# Gnd nfet
w=5 l=3

+ ad=50 pd=30 as=0 ps=0

M1206 cla4_0/and_0/b pdblock_2/and_0/a_n67_5# cla2_0/and3_0/c Gnd nfet
w=5 l=3

+ ad=55 pd=32 as=0 ps=0

M1207 cla4_0/OR5_0/vdd bc pdblock_2/and_0/a_n67_5#
pdblock_2/and_0/w_n91_n4# pfet w=5 l=3

+ ad=0 pd=0 as=0 ps=0

M1208 pdblock_2/pblock_0/not_1/vout bc
pdblock_2/pblock_0/exor2_0/a_n24_n3#
pdblock_2/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4

+ ad=136 pd=100 as=124 ps=78

M1209 pdblock_2/pblock_0/not_0/vout ac cla2_0/and3_0/c Gnd nfet w=4
l=4

+ ad=64 pd=48 as=0 ps=0

M1210 pdblock_2/pblock_0/exor2_0/a_n5_n72#
pdblock_2/pblock_0/exor2_0/a_n10_n46# pdblock_2/pblock_0/not_1/vout
Gnd nfet w=4 l=4

+ ad=52 pd=34 as=124 ps=86

M1211 pdblock_2/pblock_0/not_0/vout ac cla4_0/OR5_0/vdd
pdblock_2/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4

+ ad=64 pd=48 as=0 ps=0

M1212 pdblock_2/pblock_0/not_1/vout ac
pdblock_2/pblock_0/exor2_0/a_n36_n72# Gnd nfet w=4 l=4

+ ad=0 pd=0 as=72 ps=52

M1213 cla2_0/and3_0/c bc pdblock_2/pblock_0/not_1/vout Gnd nfet w=4
l=3

+ ad=0 pd=0 as=0 ps=0

M1214 pdblock_2/pblock_0/exor2_0/a_13_n72#
pdblock_2/pblock_0/exor2_0/a_7_n46#
pdblock_2/pblock_0/exor2_0/a_n5_n72# Gnd nfet w=4 l=5

+ ad=64 pd=40 as=0 ps=0

```

M1215 pdblock_2/pblock_0/exor2_0/a_n36_n72# bc
pdblock_2/pblock_0/exor2_0/a_13_n72# Gnd nfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1216 cla4_0/OR5_0/vdd pdblock_2/pblock_0/exor2_0/a_n10_n46#
pdblock_2/pblock_0/exor2_0/a_n24_n3#
pdblock_2/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1217 pdblock_2/pblock_0/exor2_0/a_n24_n3# ac
pdblock_2/pblock_0/not_1/vout pdblock_2/pblock_0/exor2_0/w_n66_n9#
pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1218 cla4_0/OR5_0/vdd bc pdblock_2/pblock_0/not_1/vout
pdblock_2/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0

M1219 pdblock_2/pblock_0/exor2_0/a_n24_n3#
pdblock_2/pblock_0/exor2_0/a_7_n46# cla4_0/OR5_0/vdd
pdblock_2/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=5
+ ad=0 pd=0 as=0 ps=0

M1220 pdblock_2/pblock_0/not_0/vout ac cla4_0/OR5_0/vdd
pdblock_2/pblock_0/not_0/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0

M1221 pdblock_2/pblock_0/not_0/vout ac cla2_0/and3_0/c Gnd nfet w=4
l=3
+ ad=0 pd=0 as=0 ps=0

M1222 pdblock_2/pblock_0/not_1/vout bc cla4_0/OR5_0/vdd
pdblock_2/pblock_0/not_1/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0

M1223 pdblock_2/pblock_0/not_1/vout bc cla2_0/and3_0/c Gnd nfet w=4
l=3
+ ad=0 pd=0 as=0 ps=0

M1224 cla4_0/OR5_0/E pdblock_3/and_0/a_n67_5# cla4_0/OR5_0/vdd
pdblock_3/and_0/w_n91_n4# pfet w=5 l=3
+ ad=55 pd=32 as=0 ps=0

```

M1225 pdblock_3/and_0/a_n67_5# ad cla4_0/OR5_0/vdd
pdblock_3/and_0/w_n91_n4# pfet w=5 l=3
+ ad=65 pd=36 as=0 ps=0
M1226 pdblock_3/and_0/a_n67_n42# ad cla2_0/and3_0/c Gnd nfet w=5 l=3
+ ad=65 pd=36 as=0 ps=0
M1227 pdblock_3/and_0/a_n67_5# bd pdblock_3/and_0/a_n67_n42# Gnd nfet
w=5 l=3
+ ad=50 pd=30 as=0 ps=0
M1228 cla4_0/OR5_0/E pdblock_3/and_0/a_n67_5# cla2_0/and3_0/c Gnd nfet
w=5 l=3
+ ad=55 pd=32 as=0 ps=0
M1229 cla4_0/OR5_0/vdd bd pdblock_3/and_0/a_n67_5#
pdblock_3/and_0/w_n91_n4# pfet w=5 l=3
+ ad=0 pd=0 as=0 ps=0
M1230 pdblock_3/pblock_0/not_1/vout bd
pdblock_3/pblock_0/exor2_0/a_n24_n3#
pdblock_3/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=136 pd=100 as=124 ps=78
M1231 pdblock_3/pblock_0/not_0/vout ad cla2_0/and3_0/c Gnd nfet w=4
l=4
+ ad=64 pd=48 as=0 ps=0
M1232 pdblock_3/pblock_0/exor2_0/a_n5_n72#
pdblock_3/pblock_0/exor2_0/a_n10_n46# pdblock_3/pblock_0/not_1/vout
Gnd nfet w=4 l=4
+ ad=52 pd=34 as=124 ps=86
M1233 pdblock_3/pblock_0/not_0/vout ad cla4_0/OR5_0/vdd
pdblock_3/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=64 pd=48 as=0 ps=0
M1234 pdblock_3/pblock_0/not_1/vout ad
pdblock_3/pblock_0/exor2_0/a_n36_n72# Gnd nfet w=4 l=4
+ ad=0 pd=0 as=72 ps=52
M1235 cla2_0/and3_0/c bd pdblock_3/pblock_0/not_1/vout Gnd nfet w=4
l=3
+ ad=0 pd=0 as=0 ps=0

M1236 pdblock_3/pblock_0/exor2_0/a_13_n72#
pdblock_3/pblock_0/exor2_0/a_7_n46#
pdblock_3/pblock_0/exor2_0/a_n5_n72# Gnd nfet w=4 l=5
+ ad=64 pd=40 as=0 ps=0

M1237 pdblock_3/pblock_0/exor2_0/a_n36_n72# bd
pdblock_3/pblock_0/exor2_0/a_13_n72# Gnd nfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1238 cla4_0/OR5_0/vdd pdblock_3/pblock_0/exor2_0/a_n10_n46#
pdblock_3/pblock_0/exor2_0/a_n24_n3#
pdblock_3/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1239 pdblock_3/pblock_0/exor2_0/a_n24_n3# ad
pdblock_3/pblock_0/not_1/vout pdblock_3/pblock_0/exor2_0/w_n66_n9#
pfet w=4 l=4
+ ad=0 pd=0 as=0 ps=0

M1240 cla4_0/OR5_0/vdd bd pdblock_3/pblock_0/not_1/vout
pdblock_3/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0

M1241 pdblock_3/pblock_0/exor2_0/a_n24_n3#
pdblock_3/pblock_0/exor2_0/a_7_n46# cla4_0/OR5_0/vdd
pdblock_3/pblock_0/exor2_0/w_n66_n9# pfet w=4 l=5
+ ad=0 pd=0 as=0 ps=0

M1242 pdblock_3/pblock_0/not_0/vout ad cla4_0/OR5_0/vdd
pdblock_3/pblock_0/not_0/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0

M1243 pdblock_3/pblock_0/not_0/vout ad cla2_0/and3_0/c Gnd nfet w=4
l=3
+ ad=0 pd=0 as=0 ps=0

M1244 pdblock_3/pblock_0/not_1/vout bd cla4_0/OR5_0/vdd
pdblock_3/pblock_0/not_1/w_n33_n4# pfet w=4 l=3
+ ad=0 pd=0 as=0 ps=0

M1245 pdblock_3/pblock_0/not_1/vout bd cla2_0/and3_0/c Gnd nfet w=4
l=3
+ ad=0 pd=0 as=0 ps=0

C0 cla3_0/and_0/b cla3_0/and4_0/b 3.01fF
C1 cla2_0/and3_0/c cla3_0/and_0/b 2.00fF
C2 cla2_0/and_0/b cla3_0/and4_0/b 3.16fF
C3 cla3_0/and_0/a cla2_0/and_0/b 2.34fF
C4 cla2_0/and_0/b cla2_0/and3_0/c 3.14fF
C5 cla4_0/OR5_0/vdd cla2_0/and3_0/c 3.22fF
C6 cla4_0/and4_0/b cla4_0/and4_0/c 3.71fF
C7 cla3_0/and_0/a cla3_0/and4_0/b 13.36fF
C8 cla2_0/and3_0/c cla3_0/and4_0/b 2.90fF
C9 cla2_0/and3_0/c cla4_0/and_0/b 5.10fF
C10 cla2_0/and_0/b cla4_0/and_0/a 3.08fF
C11 VDD m2_n610_n2977# 6.34fF
C12 cla4_0/and_0/a Gnd 5.54fF
C13 pdblock_3/pblock_0/not_1/vout Gnd 2.98fF
C14 bd Gnd 6.19fF
C15 pdblock_3/pblock_0/not_0/vout Gnd 3.22fF
C16 ad Gnd 3.04fF
C17 pdblock_3/pblock_0/exor2_0/w_n66_n9# Gnd 2.46fF
C18 pdblock_3/and_0/w_n91_n4# Gnd 2.17fF
C19 pdblock_2/pblock_0/not_1/vout Gnd 2.98fF
C20 bc Gnd 6.11fF
C21 pdblock_2/pblock_0/not_0/vout Gnd 3.22fF
C22 ac Gnd 3.04fF
C23 pdblock_2/pblock_0/exor2_0/w_n66_n9# Gnd 2.46fF
C24 cla4_0/and_0/b Gnd 53.04fF
C25 pdblock_2/and_0/w_n91_n4# Gnd 2.17fF
C26 cla3_0/and4_0/b Gnd 49.40fF
C27 pdblock_1/pblock_0/not_1/vout Gnd 2.98fF
C28 bb Gnd 6.21fF

C29 pdblock_1/pblock_0/not_0/vout Gnd 3.22fF
C30 ab Gnd 3.02fF
C31 pdblock_1/pblock_0/exor2_0/w_n66_n9# Gnd 2.46fF
C32 pdblock_1/and_0/w_n91_n4# Gnd 2.17fF
C33 cla2_0/and3_0/c Gnd 116.38fF
C34 pdblock_0/pblock_0/not_1/vout Gnd 2.98fF
C35 ba Gnd 6.20fF
C36 pdblock_0/pblock_0/not_0/vout Gnd 3.22fF
C37 aa Gnd 3.03fF
C38 pdblock_0/pblock_0/exor2_0/w_n66_n9# Gnd 2.46fF
C39 cla2_0/and_0/b Gnd 107.87fF
C40 pdblock_0/and_0/w_n91_n4# Gnd 2.17fF
C41 s4 Gnd 2.96fF
C42 pblock_3/not_0/vout Gnd 3.22fF
C43 m1_981_n2115# Gnd 22.32fF
C44 pblock_3/exor2_0/w_n66_n9# Gnd 2.46fF
C45 cla2_0/NOR3_0/OUTPUT Gnd 21.17fF
C46 cla2_0/NOR3_0/w_n21_25# Gnd 2.37fF
C47 cla2_0/and_0/w_n91_n4# Gnd 2.17fF
C48 cla2_0/and3_0/w_n75_n9# Gnd 2.55fF
C49 VDD Gnd 22.37fF
C50 pblock_2/not_1/vout Gnd 2.33fF
C51 pblock_2/not_0/vout Gnd 3.22fF
C52 pblock_2/exor2_0/vdd Gnd 5.39fF
C53 pblock_2/exor2_0/w_n66_n9# Gnd 2.46fF
C54 pblock_1/not_1/vout Gnd 2.33fF
C55 pblock_1/not_0/vout Gnd 3.22fF
C56 pblock_1/exor2_0/w_n66_n9# Gnd 2.46fF
C57 pblock_0/not_1/vout Gnd 2.33fF

```

C58 m1_n610_n2977# Gnd 2.50fF
C59 pblock_0/not_0/vout Gnd 3.22fF
C60 pblock_0/not_0/vdd Gnd 2.65fF
C61 pblock_0/exor2_0/w_n66_n9# Gnd 2.46fF
C62 cla3_0/and_0/w_n91_n4# Gnd 2.17fF
C63 cla3_0/and3_0/w_n75_n9# Gnd 2.55fF
C64 cla3_0/and4_0/w_n75_0# Gnd 3.50fF
C65 cla4_0/AND5_0/w_n59_n15# Gnd 6.54fF
C66 cla4_0/OR5_0/w_n38_n3# Gnd 4.09fF
C67 cla4_0/OR5_0/D Gnd 6.79fF
C68 cla4_0/and_0/w_n91_n4# Gnd 2.17fF
C69 cla4_0/and3_0/b Gnd 3.18fF
C70 cla4_0/and3_0/w_n75_n9# Gnd 2.55fF
C71 cla4_0/OR5_0/C Gnd 5.20fF
C72 cla4_0/and4_0/d Gnd 4.73fF
C73 cla4_0/and4_0/c Gnd 3.74fF
C74 cla4_0/and4_0/b Gnd 3.95fF
C75 cla4_0/and4_0/w_n75_0# Gnd 3.50fF
C76 cla4_0/OR5_0/B Gnd 2.04fF
.tran 10p 1000p
.end

```

The propagate and generate block has a vertical pitch as well as the CLA block. The sum block has a horizontal pitch.

Verilog HDL

Code:

```

module cla(a1,a2,a3,a4,b1,b2,b3,b4,s1,s2,s3,s4);
    input a0,a1,a2,a3,a4,b1,b2,b3,b4,c1;

```

```
output s1,s2,s3,s4,c5;

wire
p1,p2,p3,p4,c1,c2,c3,c4,t1,t2,t3,t4,t5,t6,t7,t8,t9,t10,t11,t12,t13,t14
,t15,t16;

xor G1(p1,a1,b1);
xor G2(p2,a2,b2);
xor G3(p3,a3,b3);
xor G4(p4,a4,b4);
and n1(g1,a1,b1);
and n2(g2,a2,b2);
and n3(g3,a3,b3);
and n4(g4,a4,b4);


//C1
assign c1=g1;


//C2
and G1(t1,p1,c1);
or G2(c2,t1,g1);


//C3
and G3(t2,p2,g1);
and G4(t3,c1,p2,p1);
or G5(c3,t3,g2);


//C4
and G6(t4,p3,g2);
and G7(t5,p3,p2,g1);
and G8(t6,p3,p2,p1,c1);
or G9(c4,t4,t5,t6,g3);
```

```
//C5
and G10(t7,p4,g3);
and G11(t8,p4,p3,g2);
and G12(t9,p4,p3,p2,g1);
and G13(t10,p4,p3,p2,p1,c1);
or G14(c5,t7,t8,t9,t10,g4);
```

```
//sum
xor W1(s1,p1,c2);
xor W2(s2,p2,c3);
xor W3(s3,p3,c4);
xor W4(s4,p4,c5);
```

```
endmodule
```

Testbench:

```
module tb;
reg c1,a1,a2,a3,a4,b1,b2,b3,b4;
wire s1,s2,s3,s4,c5;
cla
 uut(.c1(c1),.a1(a1),.a2(a2),.a3(a3),.a4(a4),.b1(b1),.b2(b2),.b3(b3),.b
4(b4),.s1(s1),.s2(s2),.s3(s3),.s4(s4),.c5(c5));
```

```
initial begin
```

```
 $dumpfile("cla.vcd");
```

```
 $dumpvars(0,tb);
```

```
 $monitor($time," A=%b%b%b%b B=%b%b%b%b Cout=%b
S=%b%b%b%b",a4,a3,a2,a1,b4,b3,b2,b1,c1,s4,s3,s2,s1);
```

```
 c1 = 1'b1;
```

```

    a1 = 1'b1;
    b1 = 1'b1;
    a2 = 1'b1;
    b2 = 1'b1;
    a3 = 1'b1;
    b3 = 1'b1;
    a4 = 1'b1;
    b4 = 1'b1;
    #2560 $finish;
end

always #5 a1 = ~a1;
always #10 b1 = ~b1;
always #20 a2 = ~a2;
always #40 b2 = ~b2;
always #80 a3 = ~a3;
always #360 b3 = ~b3;
always #420 a4 = ~a4;
always #640 b4 = ~b4;
always #1280 c1 = ~c1;

endmodule

```

